


PCB Design workshop : Guide to astable Flip-Flop Circuit

- PCB Designing is all about placing the components, routing the traces in an optimised manner on a circuit board. To do so, it is important to know and understand the circuit in hand, which will be implemented in PCB. For example, we need to know the maximum current level between two specific components, so that we can design the trace connecting them properly.
- For this Workshop purpose, we have chosen astable flip-flop/ Astable multivibrator to be implemented in PCB. Here is a simple explanation of the circuit and as well as the pre-requisite concepts.

Pre-requisite Concepts


- **R-C circuit**

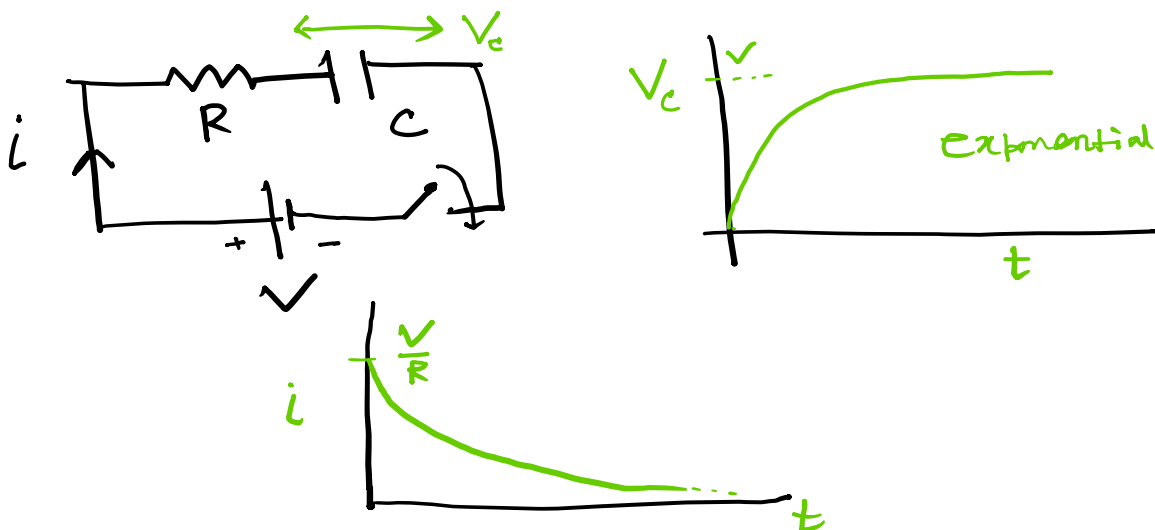For a simple R-C charging circuit as shown below , the voltage across C-capacitor



increases exponentially to reach a stable value and current decreases exponentially to reach zero.

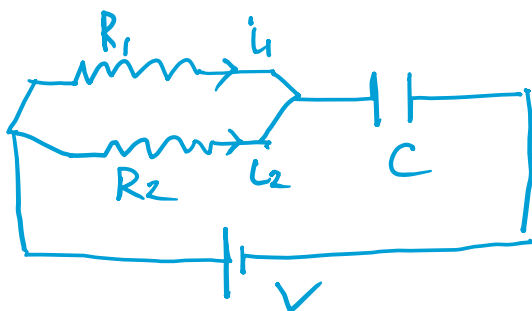In case there are multiple resistor, lower resistance path will allow more current than




$$\text{if } R_1 < R_2 \\ \text{then } i_1(t) > i_2(t)$$

higher resistance path.

let say $R_1=10\ \Omega$ and $R_2=100\Omega$, then i_1 will be 10 times i_2 .

- **Bipolar Junction Transistor as a switch**

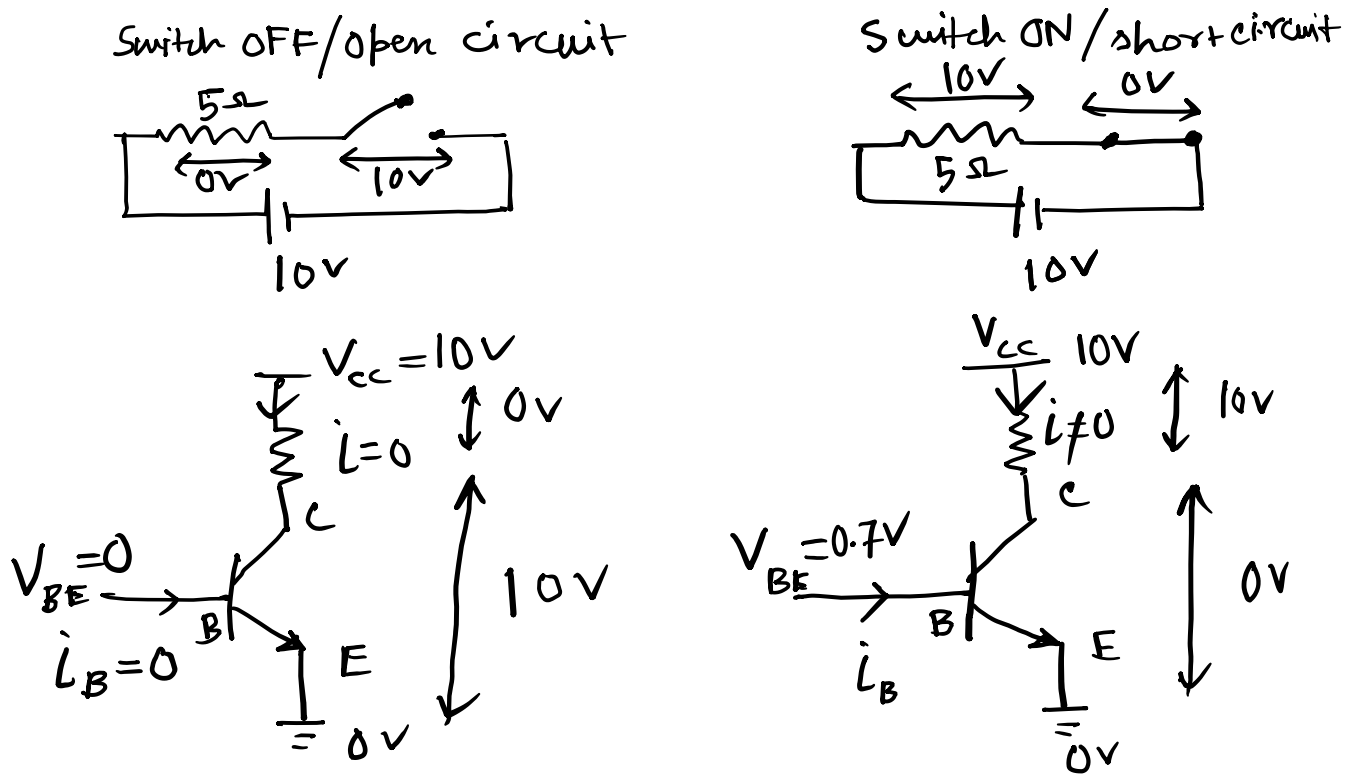
BJT is essentially a current controlled current source device. We can use it as a switch by controlling the base current. When base current I_b is zero the BJT work as open circuit and when base current is bot zero, it act as a short circuit. Note how voltage



across transistor (V_{CE}) changes in open circuit and Short circuit condition.


Astable Multivibrator

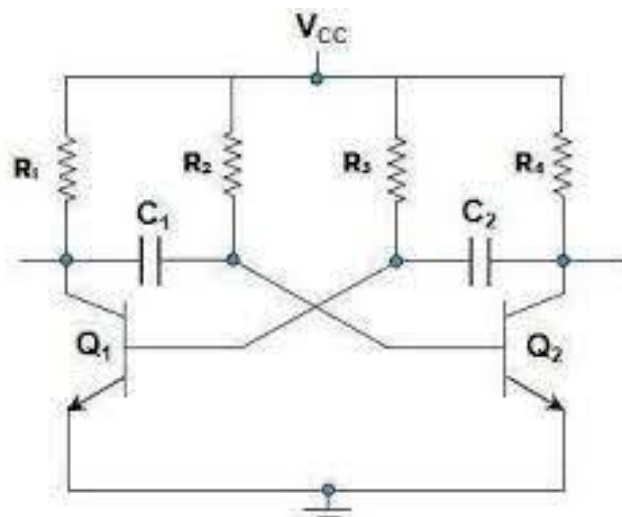A multivibrator circuit has 2 states--- High and low. Astable means none of the states are stable and continuously changing, although the input is only steady DC. The frequency of change is determined by the passive components (R and C). The circuit is as below----




So How it works?

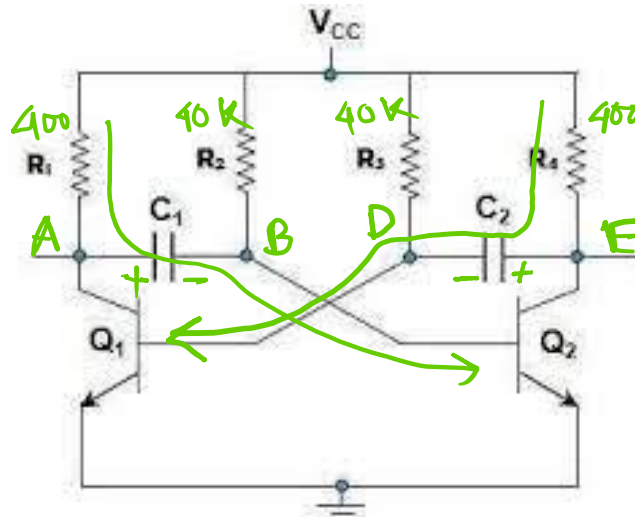- Let's assume $R_1=R_4=400\ \Omega$, $R_2=R_3=40000\ \Omega$ and $C_1=C_2=100\ \mu\text{F}$. When supply is given, both capacitors will draw current to charge up (through resistor R_1 , R_4 and not through R_2 , R_3 as they are of much higher value) and both transistors will try to turn




on. But due to inherent mismatch in transistors and circuit, only one will turn on first. Let's assume Q_1 turns on first.

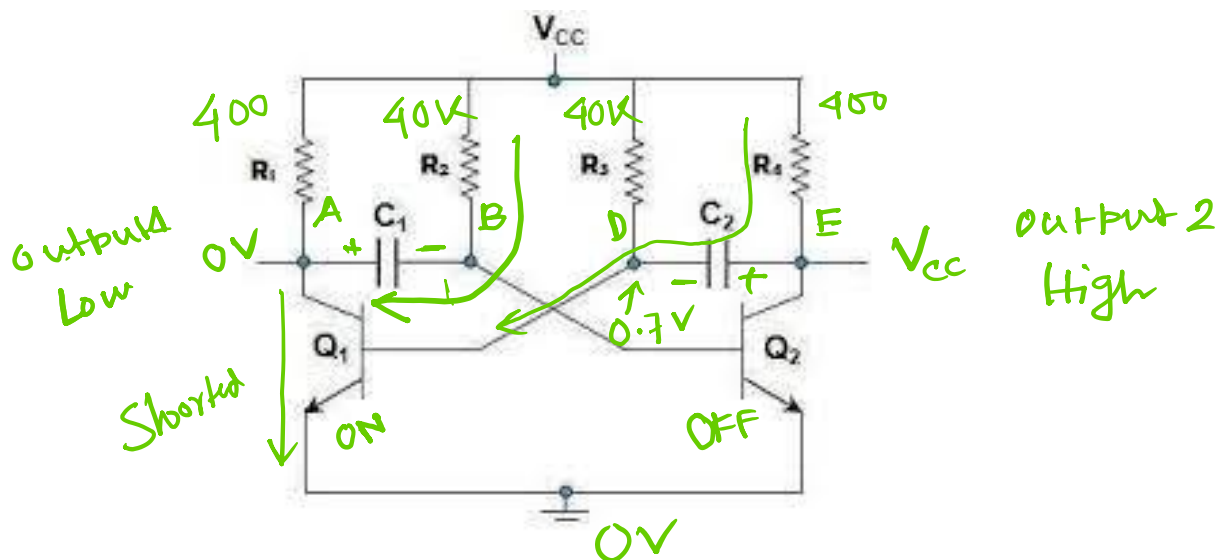- The moment Q_1 turns on, it gets shorted with ground and point A becomes grounded that is 0 volt. According to polarity of C_1 , then B must be at some negative value. And if B is at some negative value, the base of Q_2 is reverse biased, so Q_2 remains turned OFF. So voltage at E is V_{CC} . So now output1 is Low and output2 is High



- At this moment B is at some negative voltage and D is at 0.7V (As base-emitter junction of Q_1 is conducting, and we know $V_{BE} = \text{threshold value} = 0.7\text{V}$). Now that B is at negative voltage and Q_1 is shorted, C_1 will draw current in reverse direction through R_2 and the polarity across C_1 will eventually reverse.
- During reverse charging, when point B reaches 0.7V, it turns on Q_2 . The moment Q_2 turns on, point E becomes grounded and D becomes some negative voltage,

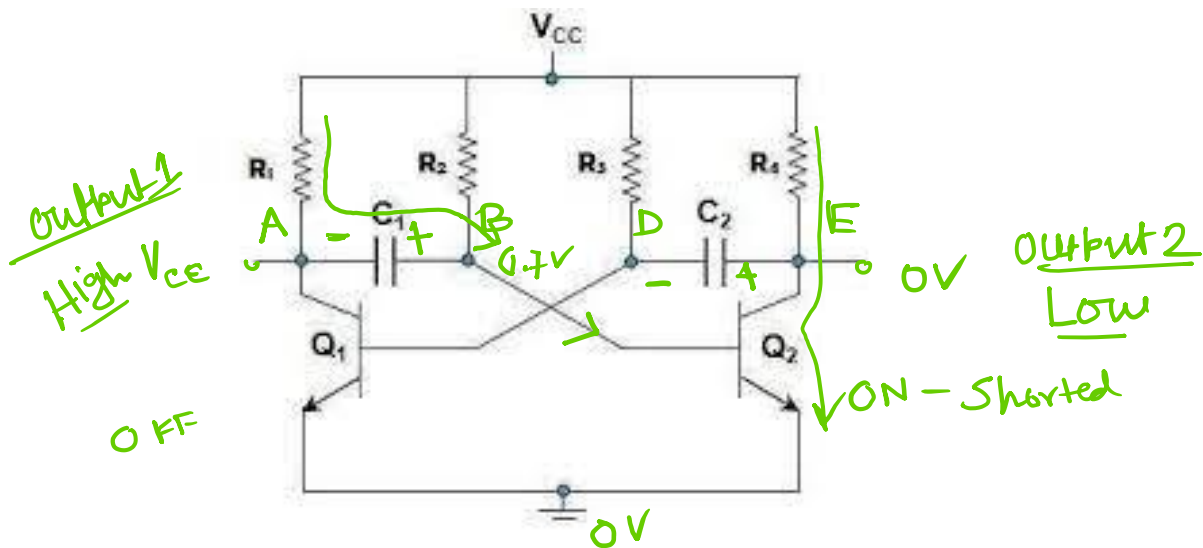stopping base current of Q1 and turning it off. So now output 1 is high and output 2 is low.



- So now, C2 will start drawing current through R3, eventually reversing its polarity and when point D reaches 0.7 V from some negative value it will turn on Q1 and turn off Q2. Thus the process will continue.

Here is some simulation result from LTSpice

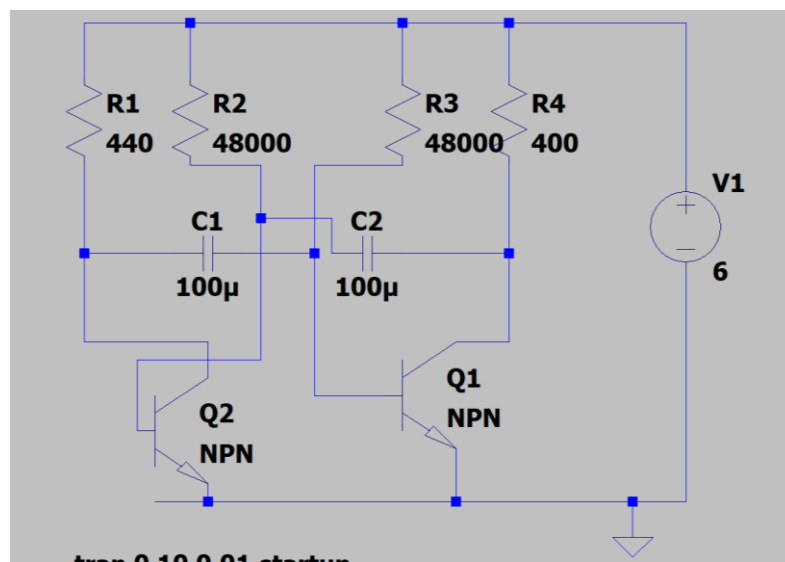


Figure 1 -Circuit of Astable Flip Flop

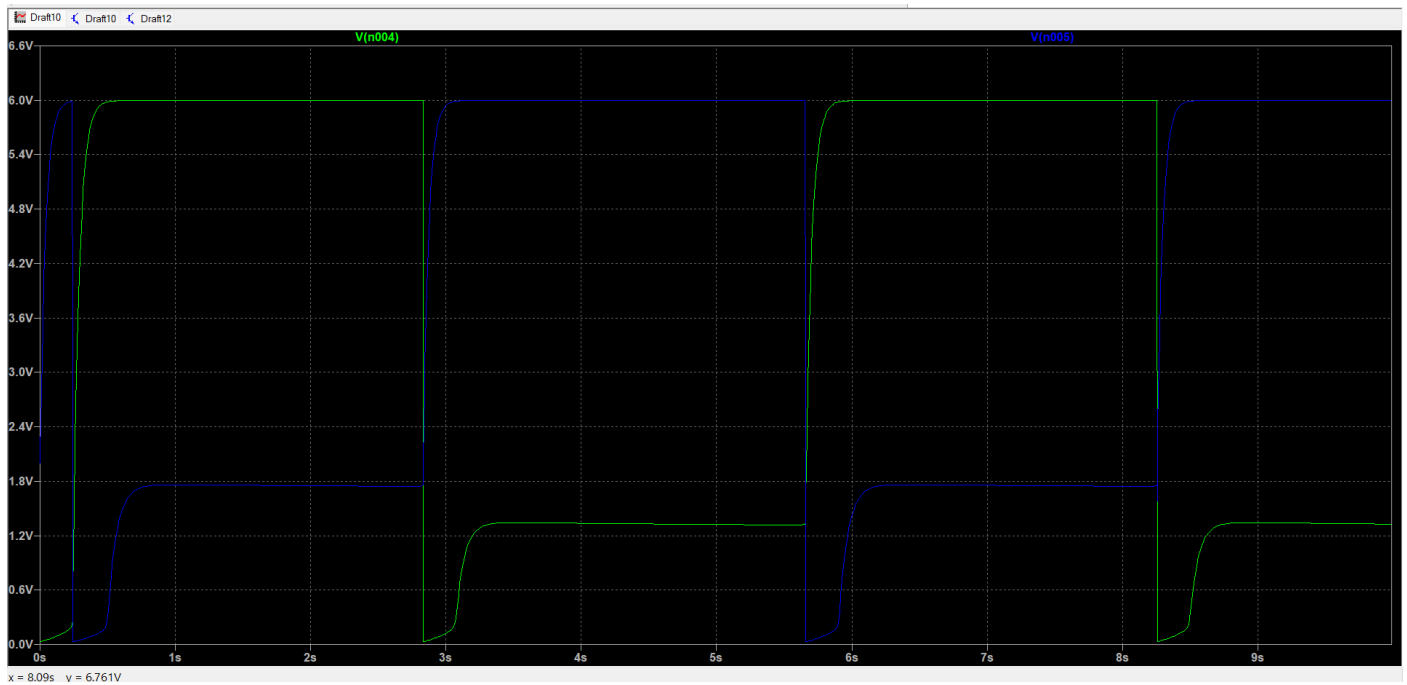


Figure 2 --Simulation result in LTSpice , green waveform is for output1 and blue for output2

References

Here is some web resources for astable flip-flop.

- https://www.tutorialspoint.com/pulse_circuits/pulse_circuits_astable_multivibrator.htm
- <https://www.electrical4u.com/astable-multivibrator/>
- https://www.youtube.com/watch?v=dQbrl_iQWig
- <https://www.youtube.com/watch?v=EZ0YZcC84m4>